




The Light Bulb Problem

Your friend Addison has just finished putting a simple circuit together using a battery, bulb, switch, and wire. After completing the circuit, the bulb does not light.

 What are two things you would suggest to Addison to try to figure out why the bulb did not light?

Use words and pictures – sketches, diagrams, drawings – to explain your thinking.

